

**NATIONAL INSTITUTE OF ELECTRONICS AND INFORMATION
TECHNOLOGY, CALICUT**



VLSI for Beginners

Verilog HDL Exercises



Contact Point for the Lab

Mr. Sreejeesh SG

Senior Technical Officer

Email: sreejeesh@nielit.gov.in

Ph.: 9447769756 (WhatsApp Preferred)

- 1. Design & test the following basic Logic Gates using Verilog HDL and capture the waveforms: a)OR, B)AND, c)NOT, d)NAND, e)XOR, f)NOR*
- 2. Design a Half Adder using Verilog HDL, Simulate and capture the waveforms in a)Dataflow modelling, b)Behavioral modelling and c)Structural modelling*
- 3. Design a Full Adder using Verilog HDL, Simulate and capture the waveforms in a)Dataflow modelling, b)Behavioral modelling and c)Structural modelling*
- 4. Design a Half Subtractor using Verilog HDL, Simulate and capture the waveforms in a)Dataflow modelling, b)Behavioral modelling and c)Structural modelling*
- 5. Design a Full Subtractor using Verilog HDL, Simulate and capture the waveforms in a)Dataflow modelling, b)Behavioral modelling and c)Structural modelling*
- 6. Design and simulate 4:1 Multiplexer using Verilog HDL and capture the waveforms*
- 7. Design and test a 4-Bit Up Counter (Synchronous) , write it's test bench and capture the waveforms in Behavioral modelling*